

# On-chip transistors extend audio amp's design flexibility

by Jim Williams  
National Semiconductor Corp., Santa Clara, Calif.


The availability of extremely low-cost audio-amplifier integrated circuits with on-chip transistor arrays, such as National's LM389, gives designers a great deal of flexibility in designing audio circuits. They make it much easier to develop low-cost versions of circuits unrelated to basic audio amplification, such as dc-dc converters, touch switches, stabilized frequency standards, scope calibrators, low-distortion oscillators, and logarithmic amplifiers. The designs of the often-needed converter, a bistable touch switch, and a tuning-fork frequency standard are discussed here in the first part of this two-part presentation.

The LM389 contains a 250-milliwatt audio amplifier

and an array of three npn transistors, each of which is uncommitted. The amp has differential inputs and separate pins for setting its gain (from 20 to 200) via a resistor and runs off a single supply that may range from 4 to 15 volts. The three transistors have a minimum current-handling capability of 25 milliamperes and a minimum current gain of 100 for  $V_{ce\ max} = 12\ v$  and for a wide range of collector currents. The chip is therefore ideal for general use.

One area in which the chip will be useful is in dc-dc switching conversion. The device in Fig. 1 is intended for use as a power supply in a digital system where it is necessary to supply  $\pm 15\ v$  to a low-power load. As can be seen from the oscilloscope photograph, the LM389 switches at 20 kilohertz. That rate is determined by the triangular-wave feedback signal, whose time constant is set by  $R_1C_2$ , and its square-wave output is applied to transistors  $Q_1$  and  $Q_3$ . The series diodes ensure clean turn-off for  $Q_1$  and  $Q_3$ .

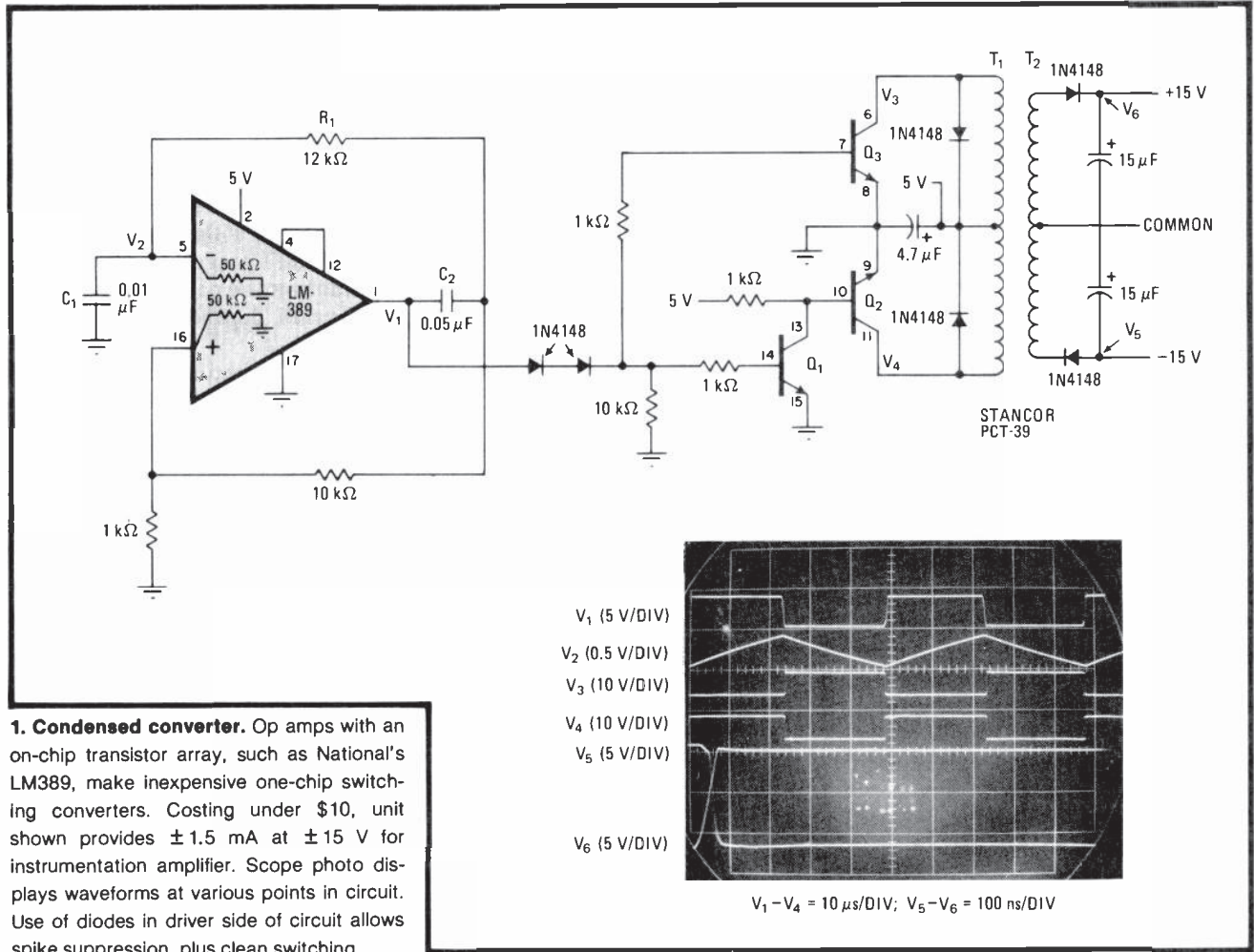$Q_1$ 's inverted output drives one half of the transformer primary through  $Q_2$ , while  $Q_3$  drives the other half. The diodes across  $Q_2$  and  $Q_3$  suppress spikes. Thus there is an





formed by  $Q_2$  and  $Q_3$ . In this manner, the output of the flip-flop changes state each time the touch plate is contacted, prompting the firing of the silicon controlled rectifier or triac that switches ac power to the load.

Figure 3 shows a tuning-fork frequency standard that is stabilized by appropriate feedback. Both sine-wave and TTL-compatible outputs are available. As the circuit needs only 5 v, it can run off a battery.

The tuning fork proper supplies a low-frequency output that is very stable (typically to within 5 ppm/ $^{\circ}$ C) and has an initial accuracy of within 0.01%. Moreover, it will withstand vibration and shock that would fracture a

quartz crystal. Here,  $Q_3$  is set up in a feedback configuration that forces the fork to oscillate at its resonant frequency.  $Q_3$ 's output is squared up by  $Q_1$  and  $Q_2$ , which provide a TTL-compatible output. When passed through an LC filter and the op amp, which provides a low-impedance (8-ohm) output, the signal is converted into a sine wave having less than 1% distortion, as shown in the figure.

Several other useful circuits also can be built. The second part of this article will deal with the chip's use in a portable scope calibrator, a low-distortion oscillator, and as a logarithmic amplifier.  $\square$

---

# On-chip transistors add versatility to op amp

by Jim Williams  
National Semiconductor Corp., Santa Clara, Calif.

Low-cost audio-amplifier chips containing uncommitted transistor arrays are widely applicable, as discussed in part 1 of this article [*Electronics*, Jan. 27, 1981, p. 118]. Besides uses in nonaudio applications such as dc-dc converters, touch switches, and stabilized frequency standards, array amplifiers like National's LM 389 are especially suited for general service in portable oscilloscope calibrators, low-distortion oscillators, and logarithmic amplifiers.

For example, the circuit in Fig. 1 allows a quick check of an oscilloscope's time base and vertical calibration. It can be built into a small hand-held enclosure and may be powered by a 12.5-volt battery.

When suitably trimmed, the amplifier will oscillate at 1 kilohertz  $\pm$  5 hertz. Transistor  $Q_1$  serves as a switch to provide fast, sharp edges to  $Q_2$ 's base. This transistor drives  $Q_3$ , which functions as a zener diode so that a relatively constant 10-v square wave is applied across the resistive divider at the output.  $Q_3$ 's breakdown potential is scaled by the 2-kilohm potentiometer to provide a 5-, a 1-, and a 0.1-v square wave at the appropriate output taps. Loading of the circuit by a 1-megohm oscilloscope impedance will not introduce any appreciable error.

In Fig. 2, the LM389 is called on to provide a low-


distortion sine wave and a synchronous in-phase square wave. The circuit's 0.25-watt output capability enables it to drive such loads as a transducer bridge. In such an application, the in-phase square-wave output can be used to drive a set of synchronous demodulation switches.

The oscillator's low distortion (0.2%) is directly traceable to the use of a light bulb that provides smooth amplitude-limiting for the Wien-bridge network of the amplifier. The oscillation frequency is 1 kHz. The in-phase square-wave output is ensured by  $Q_1$ - $Q_3$  and the potentiometer  $R_1$ , with  $Q_2$  and  $Q_3$  speeding up the waveform's edges. Calibration for synchronism is simply performed by adjusting  $R_1$  so that the edges of the square wave line up precisely with the zero-crossings of the sine-wave output.

As shown in Fig. 3, the LM389 is used in an unorthodox fashion to build a logarithmic amplifier that eliminates the complex and expensive means by which temperature compensation is usually achieved. Thus, the cost of the log amp is reduced by some 90% compared with that of conventional approaches.

$Q_2$ - $Q_3$  operate in a heat-generating and -sensing feedback network, with  $Q_2$  serving as the heater and  $Q_3$  the temperature sensor. This combination keeps the temperature virtually constant, so that the LF353 op amp's transfer function, as determined solely by logging transistor  $Q_1$  and the 1N4148 diode, will be independent of any variation in temperature.

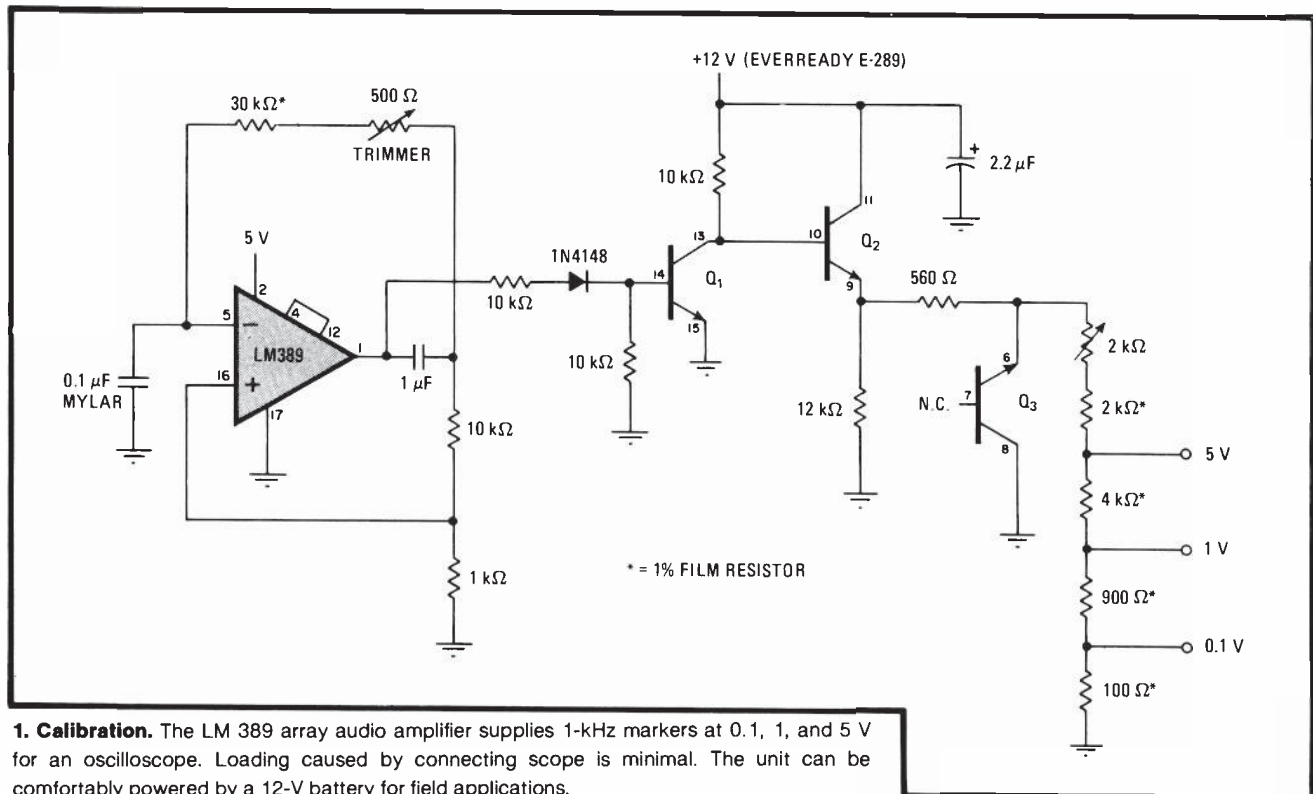When power is first applied,  $Q_2$ 's emitter voltage rises to about 3.3 v and a current of 120 milliamperes flows. This current forces  $Q_2$  to dissipate about 1.5 w, which raises the chip to operating temperature very rapidly because of its small size. At this time, the thermal servo  $Q_2$ - $Q_3$  takes over, because the LM389 senses the depen-



**1. Calibration.** The LM 389 array audio amplifier supplies 1-kHz markers at 0.1, 1, and 5 V for an oscilloscope. Loading caused by connecting scope is minimal. The unit can be comfortably powered by a 12-V battery for field applications.



